

Module 8 – Verilog

CSE-103 Digital Computer Logic

Athar Mahboob

WWW: <http://www.atharmahboob.com>

Email: athar@atharmahboob.com

Module Outline

- What is Verilog?
- Verilog modules
- Types of Verilog Code
- Verilog simulators
- Example Verilog Code
- Working with Silos

Verilog Basics

- Verilog is a HDL – Hardware Description Language
- Originated at Gateway Design Automation around 1987, later purchased by Cadence Design Systems
- The other HDL is VHDL (VHSIC-HDL)
- Originally Verilog only meant to simulate
- Later on, synthesis also added
- A subset of Verilog that can be synthesized is called RTL Verilog

Verilog Modules

- A basic entity is called a module in Verilog
- Modules have input ports and output ports
- You can instantiate modules inside other modules
- You have to write a test-bench module to test your design modules
- The test-bench module instantiates your design modules, gives them appropriate set of inputs and lets you observe the outputs of interest

Test Bench and Module Under Design/Test

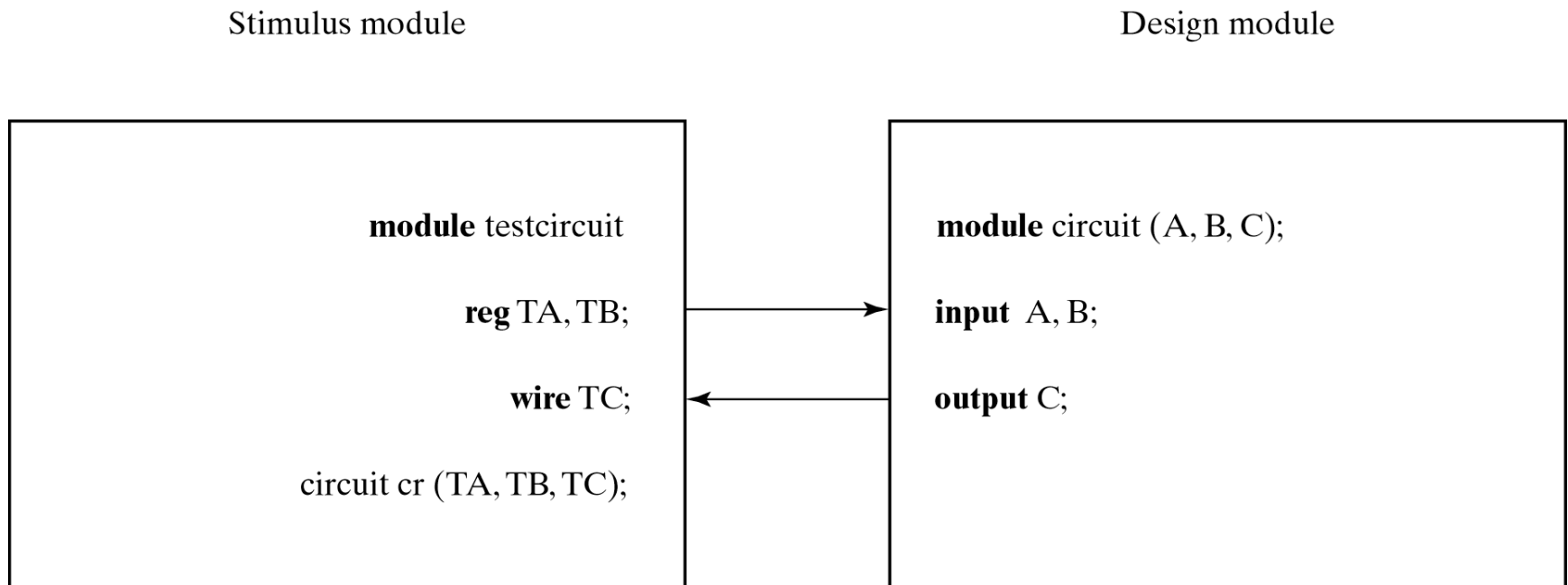


Fig. 4-33 Stimulus and Design Modules Interaction

Types of Verilog Coding

- **Behavioral** – just like a normal programming language but with the difference of time
- **Structural** – uses primitives for basic gates, etc. and connects devices much in the same way that you would on a breadboard
- **RTL Verilog** – a subset of Verilog that can be synthesized. Synthesis means automatic generation of the digital circuit based on the Verilog code. Synthesis is done using a synthesis tool

Verilog Simulators

- There are many available such as from:
 - Synopsys - VCS
 - ModelTech – Modelsim
 - Silos
 - Many others
- We shall use Silos

Example – SR Latch

```
// This is a comment
// A circuit to implement a SR Latch
//
module srlatch(s, r, q, qbar);

input s, r;
output q, qbar;

reg q, qbar;
wire s, r;

always @ (s or r)

begin

q = ~(r | qbar);
qbar = ~(s | q);

end

endmodule
```

A Test Bench for SR Latch

```
// Testbench for the SR latch
//
module tbsrlatch();

wire q, qbar;
reg s, r;

srlatch mysrlatch(s, r, q, qbar);

initial

    begin

        s = 1'b0;
        r = 1'b0;

        #10 s = 1'b1;
        r = 1'b0;
        #10 s = 1'b0;
        r = 1'b0;
```

```
        #10 s = 1'b0;
        r = 1'b1;

        #10 s = 1'b0;
        r = 1'b0;

        #10 s = 1'b1;
        r = 1'b1;

        #10 s = 1'b0;
        r = 1'b0;

        #10 s = 1'b0;
        r = 1'b1;

        #50;

        $finish;

    end

endmodule
```

Working with Silos

- A Windows-based Verilog Compiler and Simulator
- Comes with a GUI and waveform display
- Download at <http://www.simucad.com>
- Demo version password is sim2001
- You need to be connected to Internet to install it
- You create a project first and then add Verilog code files to it

Another Example

```
// verilog code for Problem 4-9
//
module posedgedflipflop(d, clock, q, qbar);

input d, clock;
output q, qbar;

wire q, qbar;
wire d, clock;

nand n1(outn1, outn4, s);
nand n2(s, outn1, clock);

nand n3(r, s, clock, outn4);
nand n4(outn4, r, d);

nand n5(q, s, qbar);
nand n6(qbar, r, q);

endmodule
```

Test Bench Another Example

```
// Testbench for the Positive Edge-
// Triggered D Flip-flop
//
module tbposedgedflipflop();

wire q, qbar;
reg d, clock;

posedgedflipflop myposedgedflipflop(d, clock, q, qbar);

initial
    begin
        d = 1'b0;
        clock = 0;

        #10 d = 1'b0;
        clock = 1;

        #10 d = 1'b1;
        clock = 0;
    end
endmodule
```

Test Bench Another Example - Continued

```
#10 d = 1'b1;  
clock = 1;  
#10d = 1'b1;  
clock = 0;  
#10 d = 1'b0;  
clock = 1;  
#10d = 1'b0;  
clock = 0;  
#10 d = 1'b0;  
clock = 1;  
#10d = 1'b1;  
clock = 0;  
#10 d = 1'b1;  
clock = 1;  
#10d = 1'b0;  
clock = 0;  
#10d = 1'b0;  
clock = 1;  
#50;  
$finish;
```

```
end  
endmodule
```

Waveform Output for Problem 4-9

